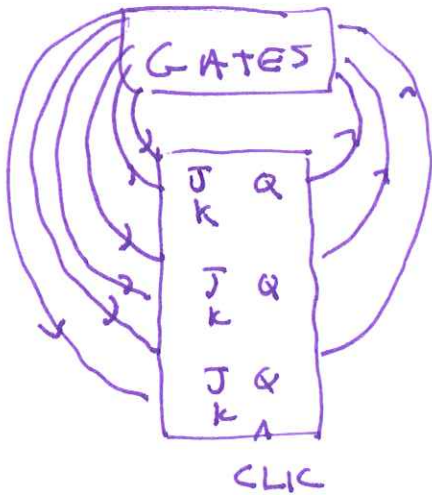


Using JKFF to "solve" state diagram problems

↳ find circuit that follows diagram



Best idea same as DFF circuits:  
GATES produce the future from present

Advantage: lots of Xs for JK make GATES a simpler circuit


transitions:

	J	K
0 → 0	0	x
0 → 1	1	x
1 → 0	x	1
1 → 1	x	0

Eg - Gray Counter: 00 → 01 → 11 → 10


Q <sub>1</sub>	Q <sub>0</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
0	0	0	x	1	x
0	1	1	x	x	0
1	1	x	0	x	1
1	0	x	1	0	x

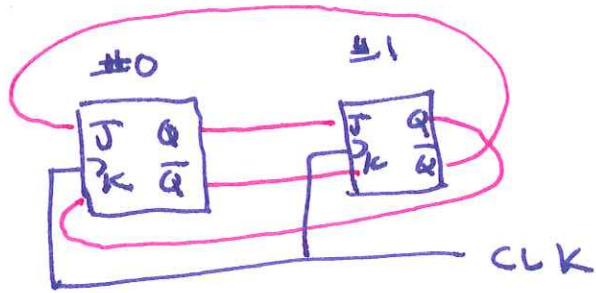Q<sub>0</sub>    Q<sub>0</sub>    Q<sub>1</sub>    Q<sub>1</sub>



often can find boolean expressions just by looking

Eg - Prime Number Counter

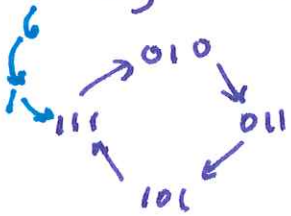

check: what happens to excluded state 6?


	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
110	0	1	1	1	1	1
001	1	0	1	1	1	0
111						

Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
0	1	0	0	x	x	0	1	x
0	1	1	1	x	x	1	x	0
1	0	1	x	0	1	x	x	0
1	1	1	x	1	x	0	x	1

Q<sub>0</sub>    Q<sub>1</sub>    Q<sub>2</sub>    Q<sub>2</sub> ⊕ Q<sub>0</sub>


Found just by looking but could k-map or heuristic if required

Eg Synchronous binary counter (3 bits)

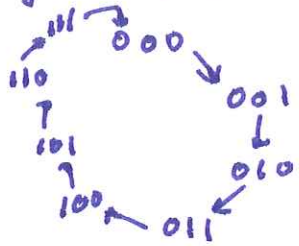


$Q_2$	$Q_1$	$Q_0$	$J_2, K_2$	$J_1, K_1$	$J_0, K_0$
0	0	0	0 X	0 X	1 Y
0	0	1	0 X	1 X	X 1
0	1	0	0 X	X 0	1 X
0	1	1	1 Y	X 1	X 1
1	0	0	X 0	0 Y	1 X
1	0	1	X 0	1 Y	X 1
1	1	0	X 0	X 0	1 X
1	1	1	X 1	X 1	X 1

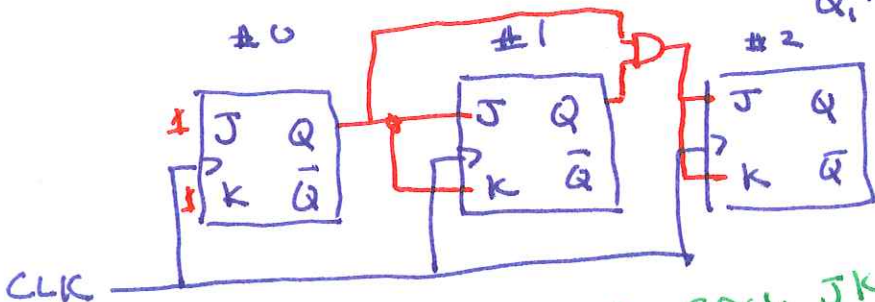$Q_2 \cdot Q_0$  (input to  $J_2$ )  
 $Q_1 \cdot Q_0$  (input to  $K_2$ )  
 $Q_0$  (input to  $J_1$ )  
 $Q_0$  (input to  $K_1$ )  
 $1$  (input to  $J_0$ )



Remark: JK FF as simple CPU; JK as "instruction"

Remark: make a DFF from JKFF

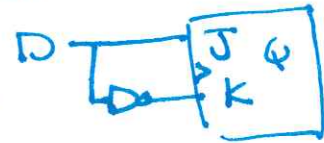

Some packaged functions

Counters - size (in bits) decade a binary

→ top count = 9; aka BCD counter

"ripple" = asynchronous or synchronous  
 up/down; carry; enables

clear, preset = load (synchronous or asynchronous)



size (in bits) - are all bits available on pins or internal)

L R shifts

clear, preset = load (synchronous or asynchronous)

use: parallel ↔ serial  
 multiply by 2