

problems: 59, 60, 73 & 61-64

59) a) if $I_D = 20 \text{ mA}$ then $V_D = 20 - 20 \text{ mA} \cdot 2 \text{ k}\Omega = -20$
 ↑ can't get \ominus from \oplus

proper: $V_D = \frac{1}{2} V_{DD} \Rightarrow 10 \text{ V}$ across $2 \text{ k}\Omega$
 $\hookrightarrow I = \frac{10 \text{ V}}{2 \text{ k}\Omega} = 5 \text{ mA}$

b) $V_G = 0$ $V_S = 5 \text{ mA} \cdot 100 \Omega = .5 \text{ V}$ $\hookrightarrow V_{GS} = -.5$ invert's

c) ~~(for high freq)~~ ~~$R_G = 100 \text{ k}\Omega$~~ $\text{Gain} = g R_D = (.01)(2000) = 20$

d) $R_G = 100 \text{ k}\Omega$

e) (for high freq) $R_D = 2 \text{ k}\Omega$

66) select $V_{DD} = 12 \text{ V}$ Q @ $V_{GS} = -.2$ & $V_{DS} = 6 \text{ V}$ & $I_D = 4.7 \text{ mA}$

$R_D = \frac{12 - 6}{4.7 \text{ mA}} = 1.3 \text{ k}\Omega$ select R_G "big" say $1 \text{ M}\Omega$

$I_D R_S = V_S = .2 \Rightarrow R_S = \frac{.2 \text{ V}}{4.7 \text{ mA}} = 43 \Omega$

$\frac{1}{\omega C_S} = \frac{1}{10} R_S \Rightarrow C_S = \frac{10}{2\pi \cdot 100 \cdot 43} = 370 \mu\text{F}$
 select freq min = 100 Hz

$\frac{1}{\omega C_{out}} = R_D \Rightarrow C_{out} = \frac{1}{\omega R_D} = \frac{1}{2\pi \cdot 100 \cdot 1300} = 1.2 \mu\text{F}$

$Z_{out} = R_D$; $Z_{in} = R_G$

$g = \frac{\Delta I_D}{\Delta V_G} = \frac{3.7 \text{ mA}}{.2 \text{ V}} = 18.5 \text{ m}\Omega^{-1}$

gain = $A_v = g R_D = -18.5 \text{ m}\Omega^{-1} \cdot 1.3 \text{ k}\Omega = -24$

73) Q @ $I_D = 3 \text{ mA}$, $V_{GS} = -1.5 \text{ V}$, $V_{DS} = 6 \text{ V}$ $V_{DD} = 12 \text{ V}$

Power = $3 \text{ mA} \cdot 6 \text{ V} = 18 \text{ mW}$

R_D (from y intercept of load line) = $2 \text{ k}\Omega$

$R_S = \frac{1.5 \text{ V}}{3 \text{ mA}} = 500 \Omega$

$g = \frac{\Delta I_D}{\Delta V_G} = \frac{2.6 \text{ mA}}{1 \text{ V}} = 2.6 \text{ m}\Omega^{-1}$

gain = $A_v = g R_D = -(2.6 \text{ m}\Omega^{-1})(2000) = -5.2$

$R_G \sim 1 \text{ M}\Omega$; $I_{DSS} = 8.5 \text{ mA}$

V_T (estimate) = -3.2 V
 $\hookrightarrow V_{APP} \rightarrow -3.8 \text{ V}$

73 more)


$$C_s = \frac{10}{\omega R_s} = \frac{10}{2\pi \cdot 100 \cdot 500} = 32 \mu F$$

$$C_{out} = \frac{1}{\omega R_D} = \frac{1}{2\pi \cdot 100 \cdot 2000} = .8 \mu F$$


$$Z_{out} \text{ (high freq)} = R_D = 2k$$

$$Z_{in} = R_C = 1M \Omega$$

61)

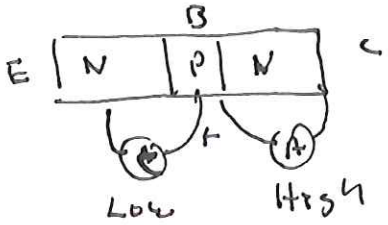

High
(back biased diode)

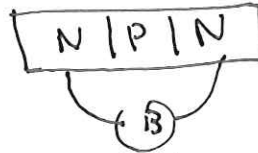

High
(one of PN junctions must be back biased)

62)

$$I_C = \frac{\Delta V}{R_C} = \frac{10 - 5}{4000} = 1.25 \text{ mA}$$

$$I_B = \frac{\Delta V}{R_B} = \frac{10 - 0.6}{100,000} = 94 \mu A$$

$$\beta = 13.3$$

$$\text{Power} = V_{CE} \cdot I_C = 5 \cdot 1.25 = 6.25 \text{ mW}$$

63) $V_{BE} = 0.6$ for any β

$$\beta = 80: \quad I_B = \frac{15 - 0.6}{200k} = 72 \mu A$$

$$I_C = 80 \cdot I_B = 5.76 \text{ mA}$$

$$V_2 = 15 - 2000 \cdot I_C = 15 - 11.5 = 3.48 \text{ V}$$

$\beta = 160$

$$I_B = \text{same}$$

$$I_C = 11.5 \text{ mA}$$

$$V_2 = 15 - 2k(11.5) < 0$$

So: This transistor is "saturated" with $V_{CE} \sim 0.2 \text{ V}$ (ie essentially zero)

$$I_C = \frac{15 - 0.2}{2000} = 7.4 \text{ mA}$$

$I_{C \text{ max}}$

↑
NOT possible

64: (left) : $V_{out} = 2.4V$ for any β

(middle)

$$3V = I_E \cdot R_E + 0.6 + I_B \cdot R_B$$

$$= ((\beta+1)R_E + R_B) I_B + 0.6$$

$$\frac{2.4}{((\beta+1)R_E + R_B)} = I_B$$

$$V_{out} = R_E I_E = R_E (\beta+1) I_B = \frac{R_E \cdot 2.4 (\beta+1)}{((\beta+1)R_E + R_B)}$$

$\beta = 50$: $\frac{3k \cdot 2.4 \cdot 51}{(51 \cdot 3k + 100k)} = 1.45V$

$\beta = 100$: $\frac{3k \cdot 2.4 \cdot 101}{(101 \cdot 3k + 100k)} = 1.80V$

(right)

$$I_B = \frac{(10 - 0.6)}{R_B} ; I_C = \beta I_B$$

$$V_{out} = 10 - R_C I_C = 10 - \frac{(10 - 0.6)}{R_B} \beta R_C$$

$\beta = 50$

$$= 10 - \underbrace{\frac{9.4}{200k} \cdot 50 \cdot 3k}_{7.05} = 2.95V$$

$\beta = 100$

$$= 10 - 2 \times 7.05 < 0 \leftarrow \text{Not possible}$$

This transistor is "saturated" with $V_{CE} \approx 0.2V$