

30-21. (a)

$$\begin{aligned}
 i &= \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) = \frac{\mathcal{E}}{2R} \\
 (1 - e^{-t/\tau}) &= \frac{1}{2} \\
 \frac{1}{2} &= e^{-t/\tau} \\
 \ln(1/2) &= -t/\tau \\
 -\ln(1/2)\tau &= t \\
 \ln(2)\frac{L}{R} &= t = \frac{\ln(2)1.25 \times 10^{-3}}{50} = 1.73 \times 10^{-5} \text{ s}
 \end{aligned}$$

(b) Since $U = \frac{1}{2}LI^2$, to have half the energy the current must be $I = i_{\max}/\sqrt{2}$

$$\begin{aligned}
 i &= \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) = \frac{\mathcal{E}}{\sqrt{2}R} \\
 (1 - e^{-t/\tau}) &= \frac{1}{\sqrt{2}} \\
 \frac{\sqrt{2} - 1}{\sqrt{2}} &= e^{-t/\tau} \\
 \ln\left(\frac{\sqrt{2} - 1}{\sqrt{2}}\right) &= -t/\tau \\
 -\ln\left(\frac{\sqrt{2} - 1}{\sqrt{2}}\right)\tau &= t \\
 -\ln\left(\frac{\sqrt{2} - 1}{\sqrt{2}}\right)\frac{L}{R} &= t = -\ln\left(\frac{\sqrt{2} - 1}{\sqrt{2}}\right)\frac{1.25 \times 10^{-3}}{50} = 3.07 \times 10^{-5} \text{ s}
 \end{aligned}$$

30-32. (a)

$$\begin{aligned}
 f &= \frac{1}{2\pi\sqrt{LC}} \\
 \sqrt{L} &= \frac{1}{2\pi f\sqrt{C}} \\
 L &= \frac{1}{(2\pi f)^2 C} = \frac{1}{(2\pi \cdot 1.6 \times 10^6)^2 \cdot 4.18 \times 10^{-12}} = 2.37 \times 10^{-3} \text{ H}
 \end{aligned}$$

(b)

$$\begin{aligned}
 f &= \frac{1}{2\pi\sqrt{LC}} \\
 \sqrt{C} &= \frac{1}{2\pi f\sqrt{L}} \\
 C &= \frac{1}{(2\pi f)^2 L} = \frac{1}{(2\pi \cdot 54 \times 10^6)^2 \cdot 2.37 \times 10^{-3}} = 37.7 \text{ pF}
 \end{aligned}$$

30-38. (a)

$$2\pi f' = \omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$
$$f' = \frac{1}{2\pi} \sqrt{\frac{1}{22 \times 10^{-3} \cdot 15 \times 10^{-9}} - \frac{75^2}{4(22 \times 10^{-3})^2}} = 8750 \text{ Hz}$$

(b)

$$A = A_0 e^{-Rt/2L}$$
$$\ln(A/A_0) = -Rt/2L$$
$$-2L \ln(A/A_0)/R = t = -2 \cdot 22 \times 10^{-3} \ln(.1)/75 = 1.35 \times 10^{-3} \text{ s}$$

(c) At critical damping $R = \sqrt{4L/C} = \sqrt{4 \cdot 22 \times 10^{-3}/15 \times 10^{-9}} = 2420 \Omega$

30-64. (a) At the instant the switch is closed the current is zero, so V_1 is zero and $V_2 = 25 \text{ V}$

(b) At long times di/dt is zero so V_2 is zero and $V_1 = 25 \text{ V}$. The current is then given by Ohm's Law $I = 25/15 = 1.67 \text{ A}$.

(c) Nothing would change.