

24-3. (a)

$$V = Q/C = \frac{.148 \times 10^{-6}}{245 \times 10^{-12}} = 604 \text{ V}$$

(b)  $C = \epsilon_0 A/d$ , so:

$$A = \frac{Cd}{\epsilon_0} = \frac{245 \times 10^{-12} \cdot .328 \times 10^{-3}}{8.8542 \times 10^{-12}} = 90.8 \times 10^{-4} \text{ m}^2$$

This would correspond, for example, to a square with side:  $s = \sqrt{90.8 \times 10^{-4}} = 9.53 \times 10^{-2} \text{ m} = 9.53 \text{ cm}$ .

(c)

$$E = \frac{V}{d} = \frac{604}{.328 \times 10^{-3}} = 1.84 \times 10^6 \text{ V/m}$$

(d)

$$\sigma = \epsilon_0 E = 8.8542 \times 10^{-12} \cdot 1.84 \times 10^6 = 1.63 \times 10^{-5} \text{ C/m}^2$$

(b) Another method of finding the area is to use the charge/(charge density):

$$A = \frac{Q}{\sigma} = \frac{.148 \times 10^{-6}}{1.63 \times 10^{-5}} = 90.8 \times 10^{-4} \text{ m}^2$$

24-7. Diameter of penny: dia=19 mm (measure or use the web); area  $A = \frac{1}{4}\pi \text{ dia}^2$

$$d = \frac{\epsilon_0 A}{C} = \frac{\frac{1}{4}\pi(19 \times 10^{-3})^2 \cdot 8.8542 \times 10^{-12}}{10^{-12}} = 2.51 \times 10^{-3} \text{ m}$$

This separation is about the thickness of two dimes together: thin but not super-thin. Deviations from the infinite plane approximation typically extend  $\pm d$  around the edge of the capacitor. Kirchhoff showed in 1877 that  $C$  is increased by fringing: approximately as if the radius of the capacitor were increased by an amount proportional to  $d$ . Here  $d$  is about 25% of the radius, so the resulting  $C$  would be noticeably larger than that calculated using the parallel plate approximation. Do note that 1 pF is quite small for a capacitor (with a result that  $d$  is unusually large): the smallest cap value we commonly stock is 10 pF, and I'd have no problem showing you a capacitor a million times bigger than that! So for reasonably sized capacitors,  $d$  would be microscopic, and the correction to the parallel plate approximation way less than 1%.

24-15. Symbolically the diagram corresponds to:  $((C_1 + C_2) \parallel C_3) + C_4$ , where  $+$  denotes series and  $\parallel$  denotes parallel. Note the simple formula valid for series combination of exactly two capacitors (product over sum):

$$C_{\text{eq}} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

For the block:  $((C_1 + C_2) \parallel C_3)$ , we have:

$$C_{\text{eq}} = \frac{C_1 \cdot C_2}{C_1 + C_2} + C_3 = \frac{C}{2} + C = \frac{3}{2} C$$

Adding in the series combination with  $C_4$  gives:

$$C_{\text{eq}} = \frac{\frac{3}{2}C^2}{\frac{5}{2}C} = \frac{3}{5}C = 2.4 \mu\text{F}$$

The charge on this equivalent capacitor (which is also the charge on  $C_4$ ):

$$Q = CV = 2.4 \times 10^{-6} \cdot 28 = 67.2 \mu\text{C}$$

The voltage drop across  $C_4$  can now be calculated:

$$V_4 = Q_4/C_4 = 67.2 \times 10^{-6}/4 \times 10^{-6} = 16.8 \text{ V}$$

Knowing  $V_4$  allows us to find the voltage drop across the  $((C_1 + C_2)||C_3)$  block:  $28 - 16.8 = 11.2 \text{ V}$ . This is of course the voltage drop across each of  $C_3$  and  $C_1 + C_2$ . The charge on  $C_3$  is then:

$$Q = CV = 4 \times 10^{-6} \cdot 11.2 = 44.8 \mu\text{C}$$

The charge on  $C_1 + C_2$  is:

$$Q = CV = 2 \times 10^{-6} \cdot 11.2 = 22.4 \mu\text{C}$$

This same charge is stored on each of  $C_1$  and  $C_2$ . The voltage drop across either of  $C_1$  and  $C_2$  can be found from this charge:

$$V = Q/C = 22.4 \times 10^{-6}/4 \times 10^{-6} = 5.6 \text{ V}$$

24-22. Symbolically the diagram corresponds to:  $10 \mu\text{F} + (5 \mu\text{F}||8 \mu\text{F}) + 9 \mu\text{F}$ , where  $+$  denotes series and  $||$  denotes parallel.

(a)

$$\frac{1}{C_{\text{eq}}} = \frac{1}{10 \mu\text{F}} + \frac{1}{5 \mu\text{F} + 8 \mu\text{F}} + \frac{1}{9 \mu\text{F}} = \frac{1}{10} + \frac{1}{13} + \frac{1}{9} = .288 \Rightarrow C_{\text{eq}} = \frac{1}{.288} = 3.47 \mu\text{F}$$

(b)

$$Q = CV = 3.47 \times 10^{-6} \cdot 50 = 174 \times 10^{-6} \text{ C}$$

(c) Same. FYI: the voltage drop across the  $10 \mu\text{F}$  is  $V = Q/C = 17.4 \text{ V}$ , the  $9 \mu\text{F}$  is  $V = Q/C = 19.3 \text{ V}$ , and the (equivalent)  $13 \mu\text{F}$  is  $V = Q/C = 13.4 \text{ V}$ ; note that these add up to the initial  $50 \text{ V}$ . If it had been requested, we could find the charge stored on the  $8 \mu\text{F}$  capacitor from:  $Q = VC = 13.4 \cdot 8 \times 10^{-6}$  (and similarly for the  $5 \mu\text{F}$  cap).