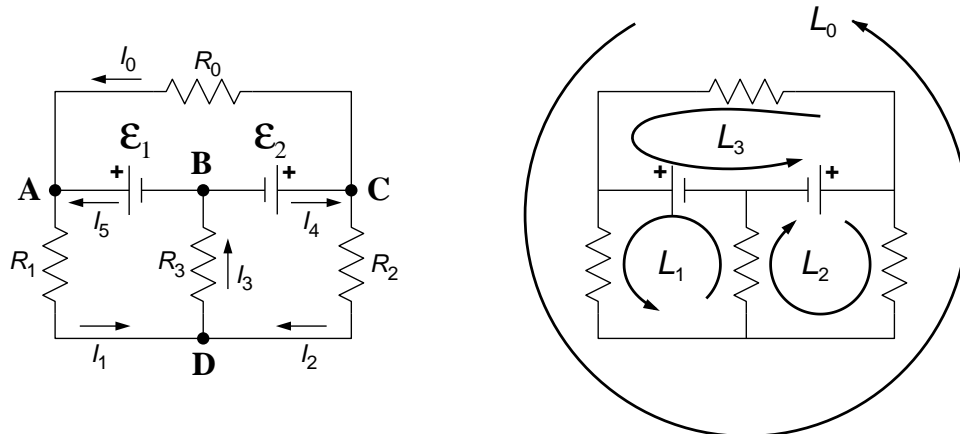


26-23. The following diagram provides generic names for the components, currents, junctions, and loops in the problem:



(a) Using the junction rule at junction **D**:

$$I_1 + I_2 = I_3 = 3 + 5 = 8 \text{ A}$$

Note that we can quickly find the other unknown currents using different junctions. Using junction **A**:

$$I_0 + I_5 = I_1 \Rightarrow I_5 = I_1 - I_0 = 1 \text{ A}$$

Using junction **C**:

$$I_4 = I_2 + I_0 = 5 + 2 = 7 \text{ A}$$

Junction **B** provides a check:

$$I_3 = I_4 + I_5 \Rightarrow 8 = 7 + 1$$

(b) Using loop L_1 :

$$\begin{aligned} \mathcal{E}_1 - I_1 R_1 - I_3 R_3 &= 0 \\ \mathcal{E}_1 &= I_1 R_1 + I_3 R_3 = 3 \cdot 4 + 8 \cdot 3 = 36 \text{ V} \end{aligned}$$

Using loop L_2 :


$$\begin{aligned} \mathcal{E}_2 - I_2 R_2 - I_3 R_3 &= 0 \\ \mathcal{E}_2 &= I_2 R_2 + I_3 R_3 = 5 \cdot 6 + 8 \cdot 3 = 54 \text{ V} \end{aligned}$$

(c) Using L_0 :

$$\begin{aligned} -I_0 R_0 - I_1 R_1 + I_2 R_2 &= 0 \\ -I_1 R_1 + I_2 R_2 &= I_0 R_0 \\ \frac{-I_1 R_1 + I_2 R_2}{I_0} &= R_0 = \frac{-3 \cdot 4 + 5 \cdot 6}{2} = 9 \Omega \end{aligned}$$

Remark: This problem is a bit unusual: typically \mathcal{E} s are known and I s are unknown (as in the lab, \mathcal{E} is easier to measure than I). In any case, Kirchhoff rules will do the trick.

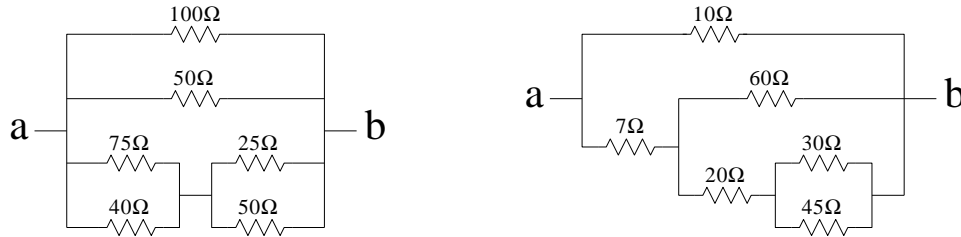26-59. It is important to realize that you can move the wires to produce more obvious circuits as shown below:



(a) Symbolically this circuit is: $100 \parallel 50 \parallel [(75 \parallel 40) + (25 \parallel 50)]$. Working through the block \square :

$$\frac{75 \cdot 40}{75 + 40} + \frac{25 \cdot 50}{25 + 50} = 42.754 \Omega$$

The parallel combination of three yields:

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{100} + \frac{1}{50} + \frac{1}{42.754} = 0.05339 \Omega^{-1} \\ R_{eq} &= 18.7 \Omega \end{aligned}$$

(b) Symbolically this circuit is: $10 \parallel \left[7 + \left(60 \parallel \{ 20 + 30 \parallel 45 \} \right) \right]$. Working through the block $\{ \}$:

$$20 + \frac{30 \cdot 45}{30 + 45} = 38 \Omega$$

Working through the block \square :

$$7 + \frac{60 \cdot 38}{60 + 38} = 30.265 \Omega$$

and finally:

$$\frac{10 \cdot 30.265}{10 + 30.265} = 7.52 \Omega$$

13. (old exam) Symbolically this circuit is: $1k + \{7k \parallel (2k + 3k + 2k)\} + 5k$. See that the $\{\}$ block: is $7k \parallel 7k = 3.5k$, so the result is $1k + 3.5k + 5k = 9.5k\Omega$. The current through the battery is $I = V/R = 15/9.5 = 1.58$ mA. The voltage drop across the $\{7k \parallel (2k + 3k + 2k)\}$ is $15 - (1 + 5) \cdot 1.58 = 5.53$ V. The current through $(2k + 3k + 2k)$ is $I = V/R = 5.53/7 = .789$ mA; this same current goes through the $3k\Omega$ resistor.
14. (old exam) Using currents in mA and resistances in $k\Omega$ (as $m \times k = 1$):

$$\begin{aligned} I_1 &= I_2 + I_3 \\ 15 - 2I_1 - 3I_2 - 5 - 5I_2 &= 0 \\ 15 - 2I_1 - 7I_3 &= 0 \\ -5 - 5I_2 + 7I_3 - 3I_2 &= 0 \end{aligned}$$

I'll use the top three equations:

$$\begin{aligned} 0 &= -I_1 + I_2 + I_3 \\ 10 &= 2I_1 + 8I_2 \\ 15 &= 2I_1 + 7I_3 \end{aligned}$$

I hope you will enter these equations into your calculator to find a solution. I'll proceed the long way: eliminate I_3 from the last equation using the first: $I_3 = I_1 - I_2$:

$$\begin{aligned} 10 &= 2I_1 + 8I_2 \\ 15 &= 9I_1 - 7I_2 \end{aligned}$$

Multiplying the top equation by 4.5 produces equal coefficients of I_1 :

$$\begin{aligned} 45 &= 9I_1 + 36I_2 \\ 15 &= 9I_1 - 7I_2 \end{aligned}$$

Now subtract:

$$\begin{aligned} 30 &= 43I_2 \\ \frac{30}{43} &= I_2 = .698 \text{ mA} \end{aligned}$$

Given I_2 we can substitute into any of the loop equations, e.g.:

$$\begin{aligned} 10 &= 2I_1 + 8I_2 = 2I_1 + 8 \frac{30}{43} \\ 10 - \frac{240}{43} &= 2I_1 \\ \frac{430 - 240}{43 \cdot 2} = \frac{95}{43} &= I_1 = 2.21 \text{ mA} \end{aligned}$$

Then $I_3 = I_1 - I_2 = 65/43 = 2.21 - .698 = 1.51$ mA. It's always wise to check your work; I'll check the bottom equation:

$$-5 - 5I_2 + 7I_3 - 3I_2 = -5 - 8I_2 + 7I_3 = -5 - 8 \times .698 + 7 \times 1.51 = -10.584 + 10.570 = -.014 \approx 0$$